

Microprocessors & Interfacing

Input/Output Devices (I)



Lecturer : Annie Guo

Lecture Overview

- Input devices
 - Push Button
 - Input switch
 - Keypad

Push Button

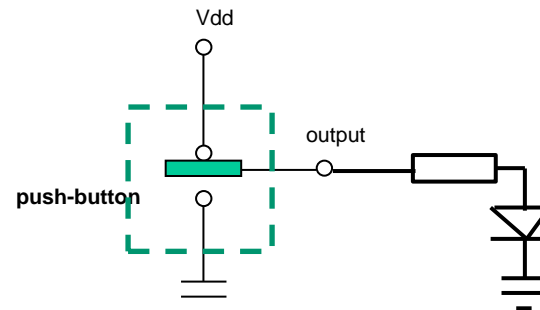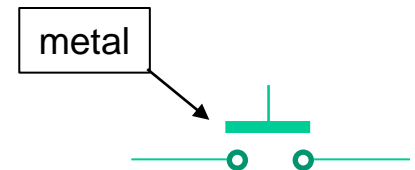
- A small mechanical device that can control the connection of two electric nodes (wires).
 - When it is pushed, the small metal inside the button connects two wires.
- Can be used as a 1-bit input device, as used in our lab board
 - Not pushed: 1
 - Pushed down: 0




Input Switch

- Like the push button, a switch provides two different values, depending on the switch position.
- Pull-up resistor/circuit may be needed for the switch to provide a high logic level when the switch is open.
- Problem with switch (also push button):
 - Switch bouncing^{弹跳}
 - When a switch makes contact, its mechanical^{弹性} springiness will cause the contact to bounce, namely contact and break, for a few milliseconds (typically 5 to 10 ms).

Switch Bouncing Example

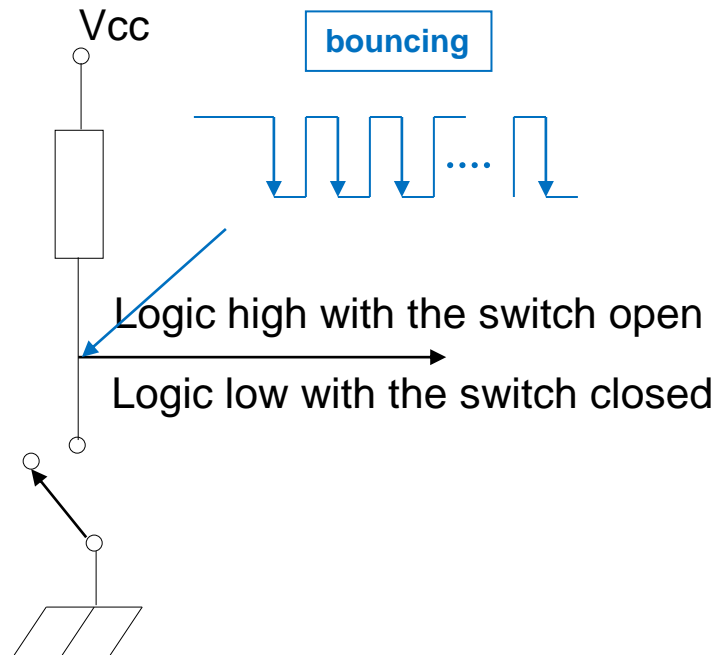


NAND Latch Debouncer*

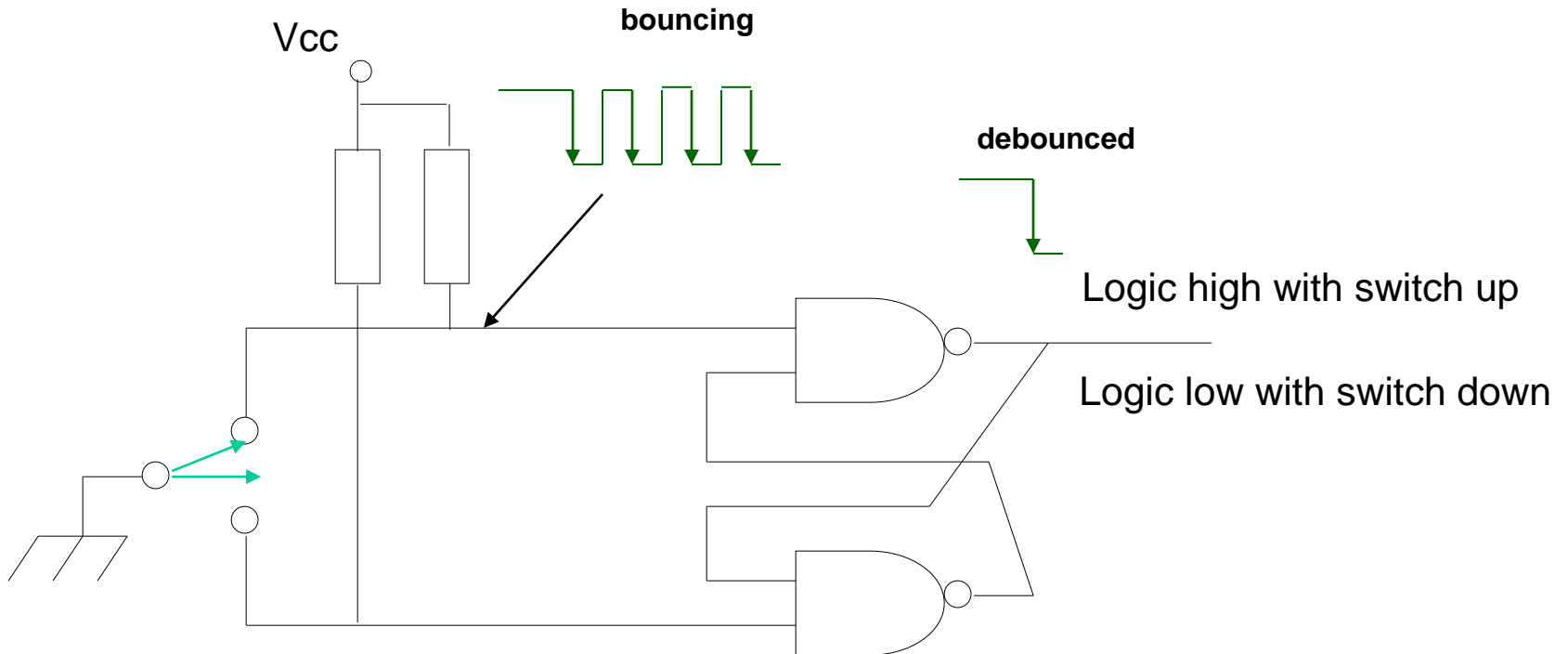

Software Debouncing

- Basic idea: wait until the switch is stable
- For example:
 - Wait and see:
 - If the software detects a low logic level, indicating that switch has closed, it simply waits for some time, say 20 to 100ms, and then tests if the switch is still low.
 - Counter-based approach:
 - Initialize a counter to 10.
 - 查询 Poll the switch every millisecond until the counter is either 0 or 20.
 - If the switch output is low, decrease the counter; otherwise, increment the counter.
 - If the counter is 0, we know that switch output has been low (closed) for at least 10 ms. If, on the other hand, the counter reaches 20, we know that the switch output has been high for at least 10 ms.

One-Dimensional Array of Switches

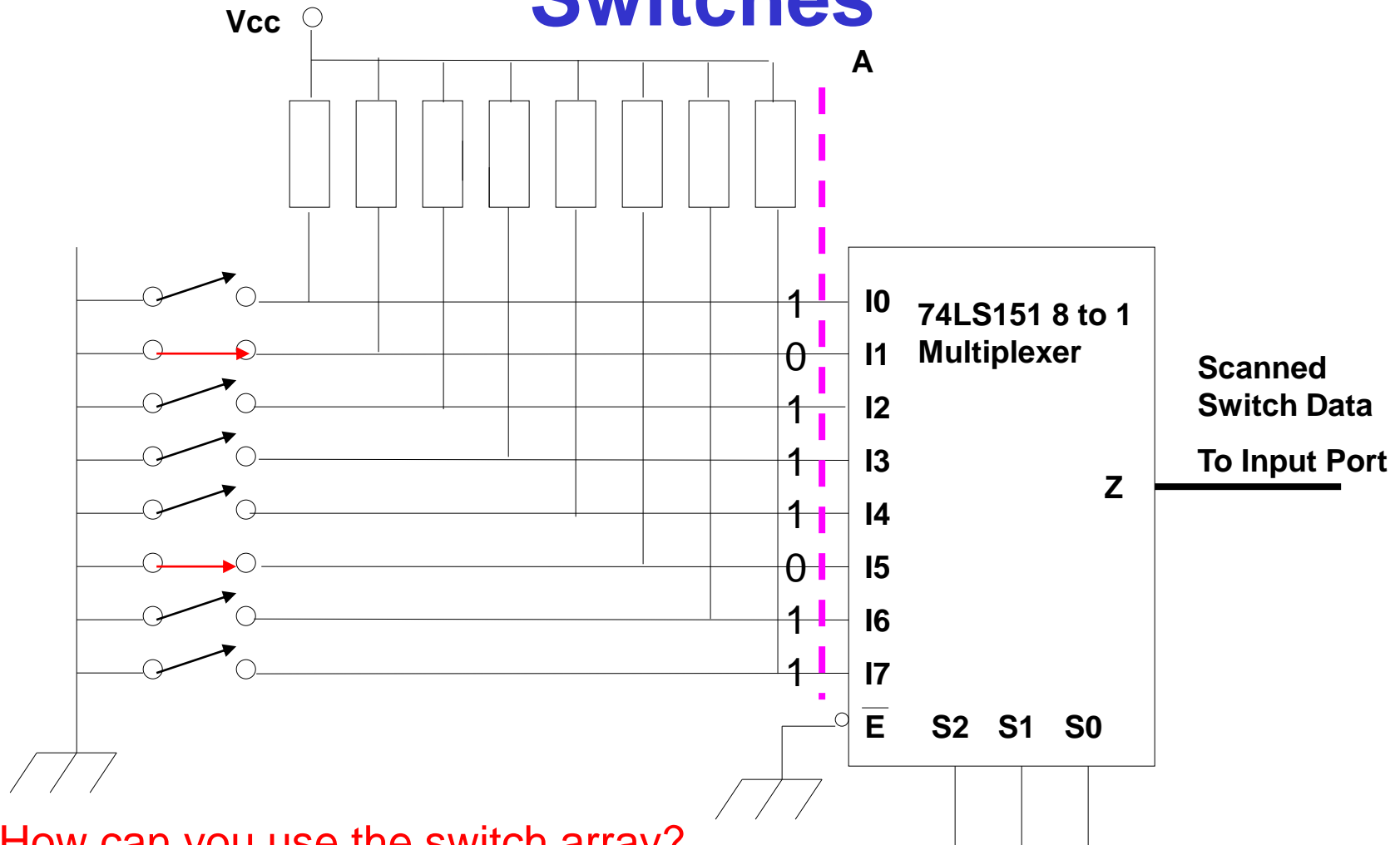

How can you use the switch array?


- get all bits from each bit line
- scan each bit in a sequence

One-Dimensional Array of Switches (cont.)

- Switch bouncing problem must be solved
 - Either using software or hardware
- The output of switch array can be interfaced directly to an eight-bit port at point A.
- The array of switches can also be scanned by the software to find out which switches are closed or open.
 - The software outputs a 3-bit sequence from 000 to 111 and the multiplexer selects each of the switch inputs.

Keypad

- Internal circuit diagram

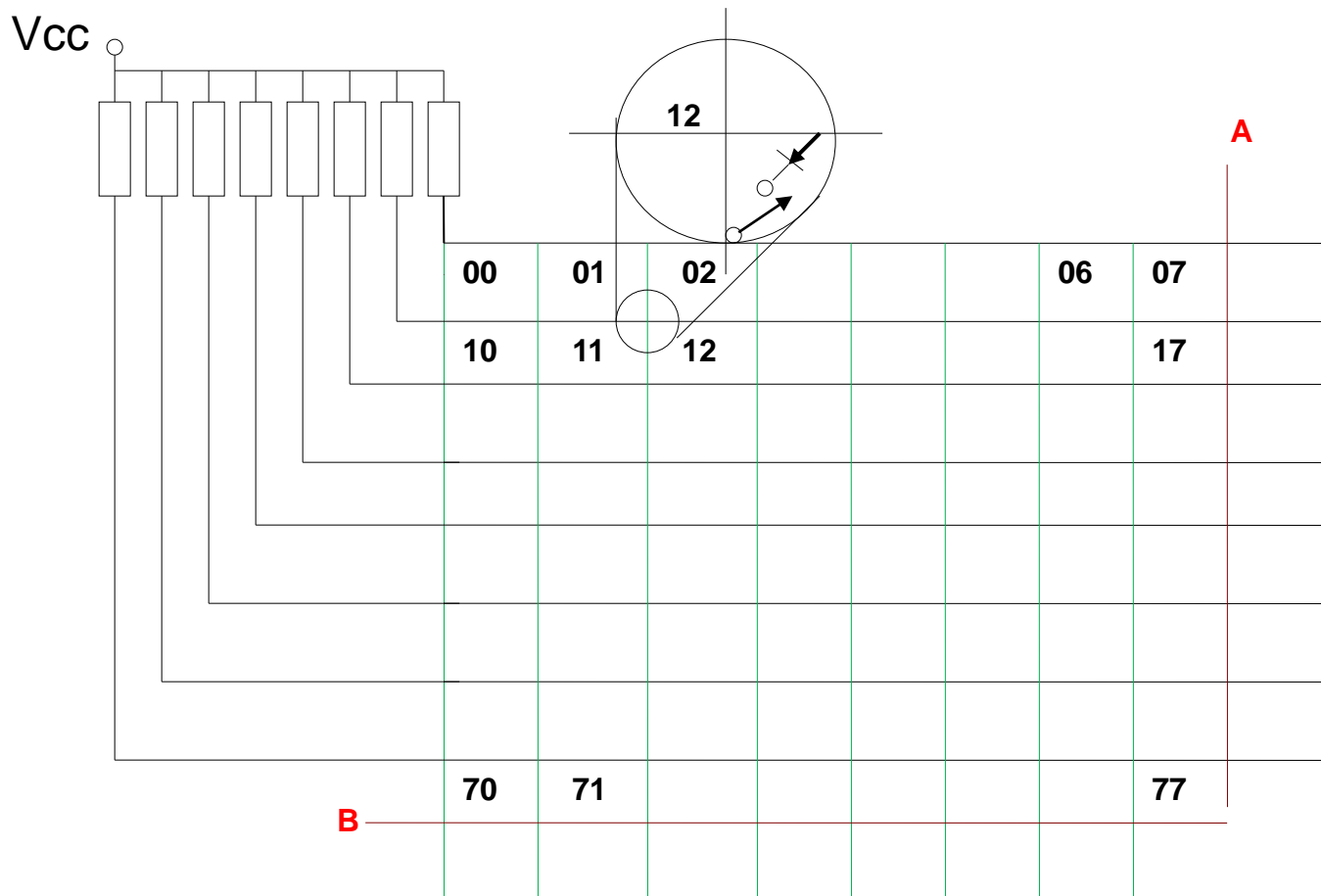

Keypad (cont.)


- A keypad is a set of switches arranged in a two-dimensional matrix, consisting of two layers
 - A layer of the horizontal lines
 - connected to the power supply via resistors
 - A layer of the vertical lines
 - normally disconnected to the horizontal layer
- Each intersection of the vertical and horizontal lines forms a switch
 - The switch can be operated by a key button
 - When the key is pressed, the switch connects both two lines.

Keypad (cont.)

- The 8*8 keypad can be interfaced directly to 8-bit output and input ports
 - at point *A* (to input port) and point *B* (to output port)
- The output from each horizontal line
 - Normally is a logic high (1)
 - Becomes logic low (0) when a key is pressed and the related vertical line is set/connected to logic low (0)
- The diode prevents a problem called **ghosting**.

What happens to the output for a key press if the related vertical line is not connected to logic low?

Ghosting*

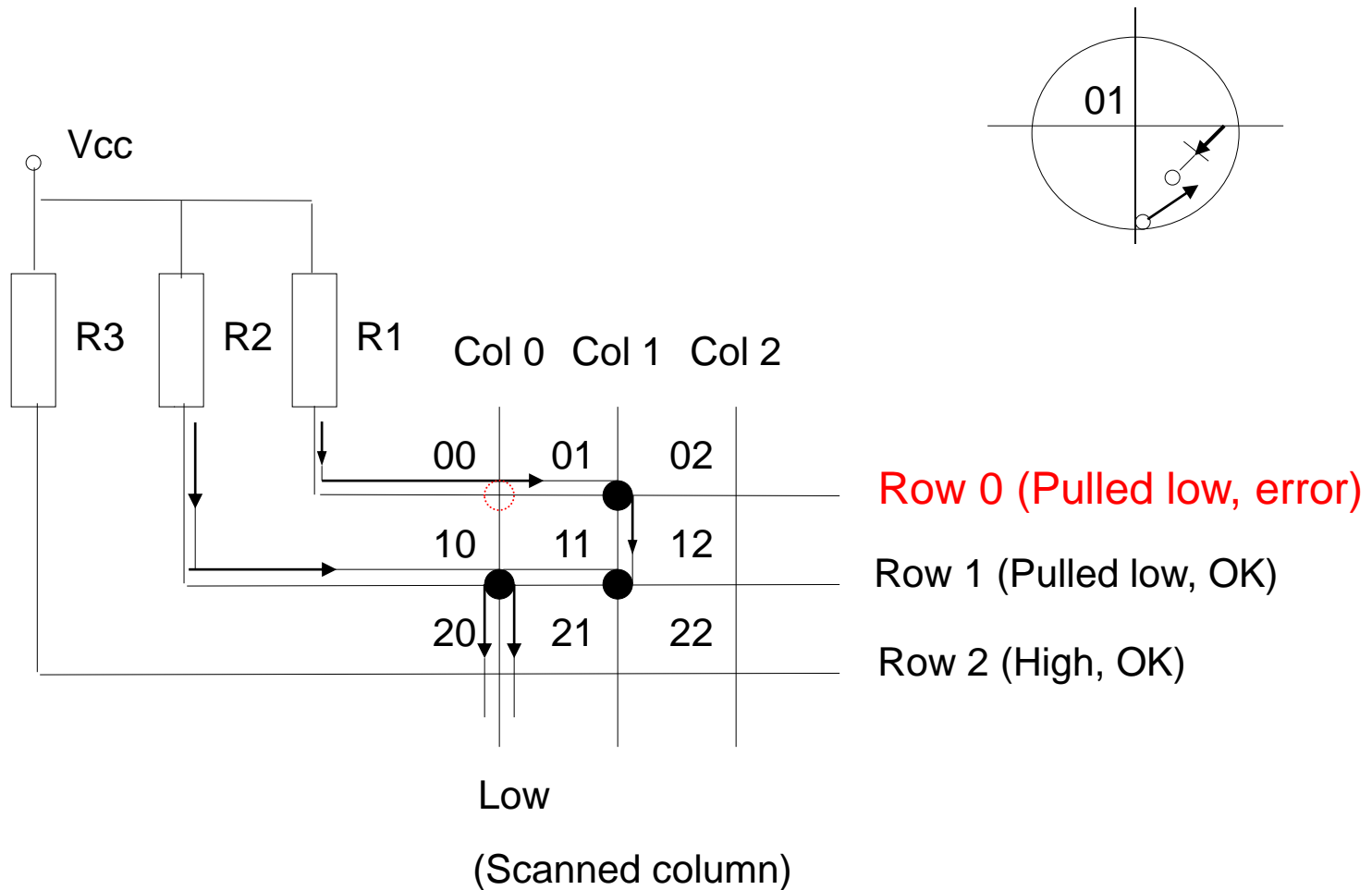


Ghosting (cont.)*

- Ghosting occurs when several keys are pushed at once.
- Consider the case shown in the figure in the previous slide, where three switches 01, 10 and 11 are all closed. Column 0 is selected with a logic low and assume that the circuit does not contain the diodes. As the rows are scanned, a low is sensed on Row 1, which is true because switch 10 is closed. But a low is also seen on Row 0, indicating switch 00 is closed, which is NOT true.
- The diodes in the switches eliminate this problem by preventing current flow from R1 through switches 01 and 11. Thus Row 0 will not be low when it is scanned.

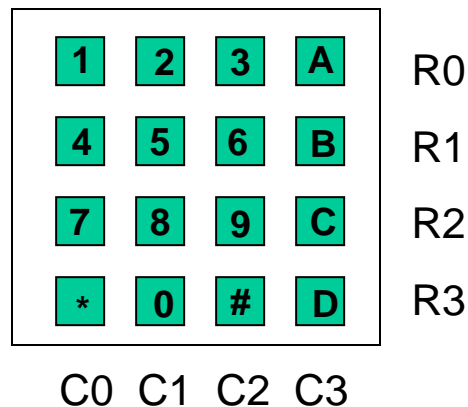Example

- Get an input from 4x4 keypad used in our lab board.



Example (solution)


- Algorithm

```
Scan columns from left to right
  for each column, scan rows from top to bottom
    for each key being scanned
      if it is pressed
        display
        wait
      endif
    endfor
  endfor
Repeat the scan process
```

- To select a column, set the related Cx value to 0
- A mask is used to read one row at a time.

Example (solution)

- Hardware Interfacing

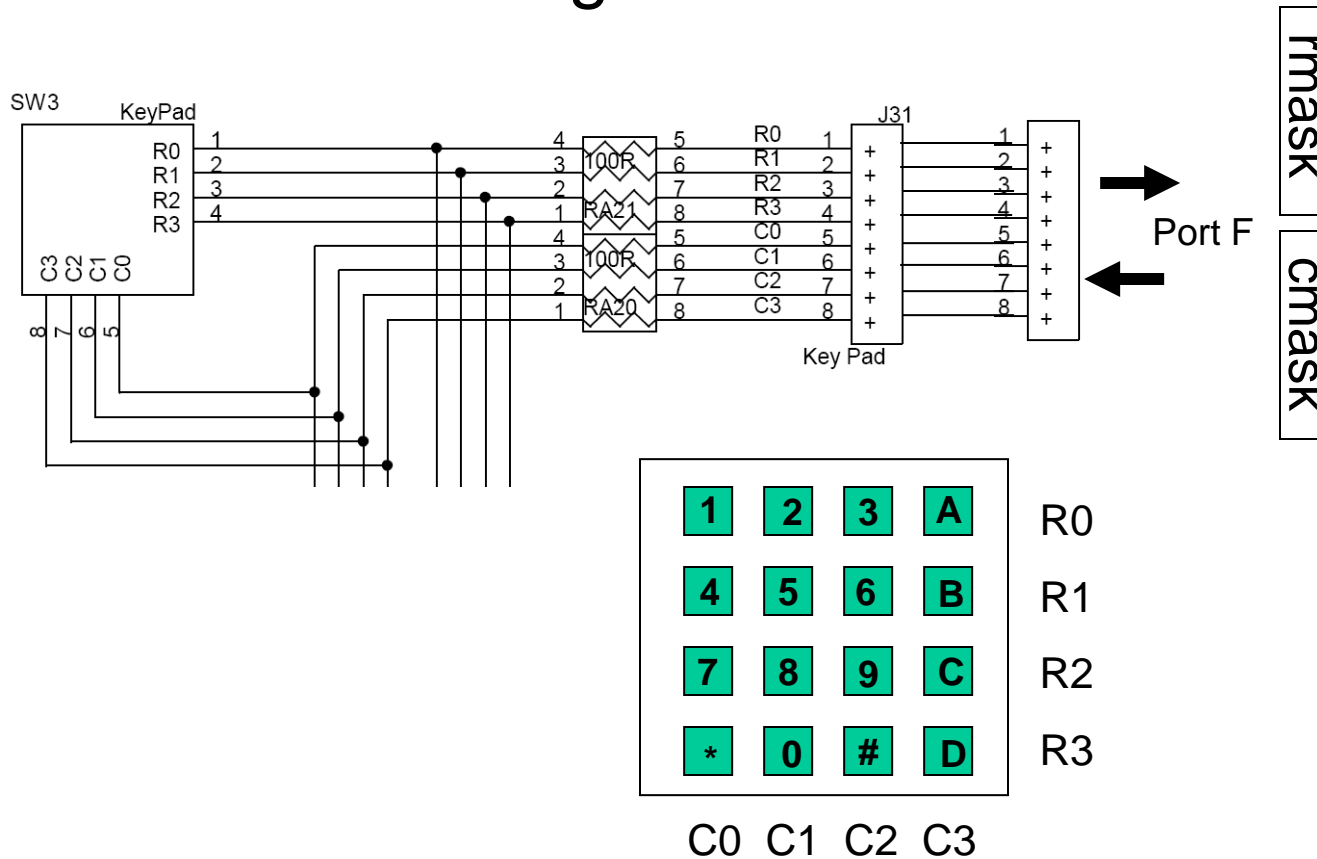

Code Implementation

; The program gets input from keypad and displays its ascii value on the
; LED bar

.include "m2560def.inc"

.def row = r16

; current row number

.def col = r17

; current column number

.def rmask = r18

; mask for current row during scan

.def cmask = r19

; mask for current column during scan

.def temp1 = r20

.def temp2 = r21

.equ PORTFDIR = 0xF0

; PF7-4: output, PF3-0, input

.equ ROWMASK = 0x0F

; for obtaining input from Port F

.equ INITCOLMASK = 0xEF

; scan from the leftmost column,

.equ INITROWMASK = 0x01

; scan from the top row

Code Implementation

RESET:

ldi	temp1, PORTFDIR	; PF7:4/PF3:0, out/in
out	DDRF, temp1	
ser	temp1	; PORTC is set output
out	DDRC, temp1	; to display ASCII of pressed.
out	PORTC, temp1	; Initially LEDs are turned on

main:

ldi	cmask, INITCOLMASK	; initial column mask
clr	col	; initial column

Code Implementation

colloop:

```
    cpi    col, 4
    breq   main
    out    PORTF, cmask
```

; if all keys are scanned, repeat.
; otherwise, scan a column

```
delay:    ldi    temp1, 0xFF
          dec    -1 temp1
          brne   delay    不相等转移
```

; slow down the scan operation.

```
    in     temp1, PINF
    andi   temp1, ROWMASK    与立即数
    cpi    temp1, 0xF
    breq   nextcol
```

; read PORTF
; get the keypad output value
; check if any row is low low:pressed, 0

```
    ldi    rmask, INITROWMASK
    clr    row
```

; if yes, find which row is low
; initialize for row check
;

Code Implementation

rowloop:

```
;cpi    row, 4
;breq   nextcol
mov     temp2, temp1
and     temp2, rmask
breq    convert
inc     row
lsl     rmask
rjmp    rowloop
```

; the row scan is over.

; check un-masked bit

; if bit is clear, the key is pressed

; else move to the next row

nextcol:

```
lsl cmask
inc col
rjmp colloop
```

; if row scan is over

; increase column value

; go to the next column

Code Implementation

convert:

cpi	col, 3	; If the pressed key is in col. 3
breq	letters	; we have a letter
		; If the key is not in col. 3 and
cpi	row, 3	; if the key is in row3,
breq	symbols	; we have a symbol or 0
mov	temp1, row	; Otherwise we have a number in 1-9
lsl	temp1	
add	temp1, row	;
add	temp1, col	; temp1 = row*3 + col
subi	temp1, -'1'	; Add the value of character '1'
rjmp	convert_end	

Code Implementation

letters:

```
ldi temp1, 'A'  
add temp1, row           ; Get the ASCII value for the key  
rjmp convert_end
```

symbols:

```
cpi col, 0                ; Check if we have a star  
breq star  
cpi col, 1                ; or if we have zero  
breq zero  
ldi temp1, '#'           ; if not we have hash  
rjmp convert_end
```

star:

```
ldi temp1, '*'           ; Set to star  
rjmp convert_end
```

zero:

```
ldi temp1, '0'           ; Set to zero
```

convert_end:

```
out PORTC, temp1         ; Write value to PORTC  
;delay  
rjmp main                ; Restart main loop
```

Reading Material

- Chapter 9: Computer Buses and Parallel Input and Output. Microcontrollers and Microcomputers by Fredrick M. Cady.
 - Simple I/O Devices

Homework

1. Refer to the AVR Instruction Set manual, study the following instructions:
 - Arithmetic and logic instructions
 - lsr, ror
 - lsl, rol
 - Data transfer instructions
 - sts, lds
 - Bit
 - clc
 - sec

Homework

2. Write an AVR assembly program to map the number-keys on the keypad to the individual LEDs on the LED bar. For example, when key 0 is pressed, LED 0 is turned on. After all number keys are pressed, all LEDs are on.