

# Microprocessors & Interfacing


## *Parallel Input/Output*

Lecturer : Annie Guo

# Lecture Overview

- I/O Addressing
  - Memory mapped I/O
  - Separate I/O
- Parallel Input/Output
  - AVR examples

# Typical Computer Structure

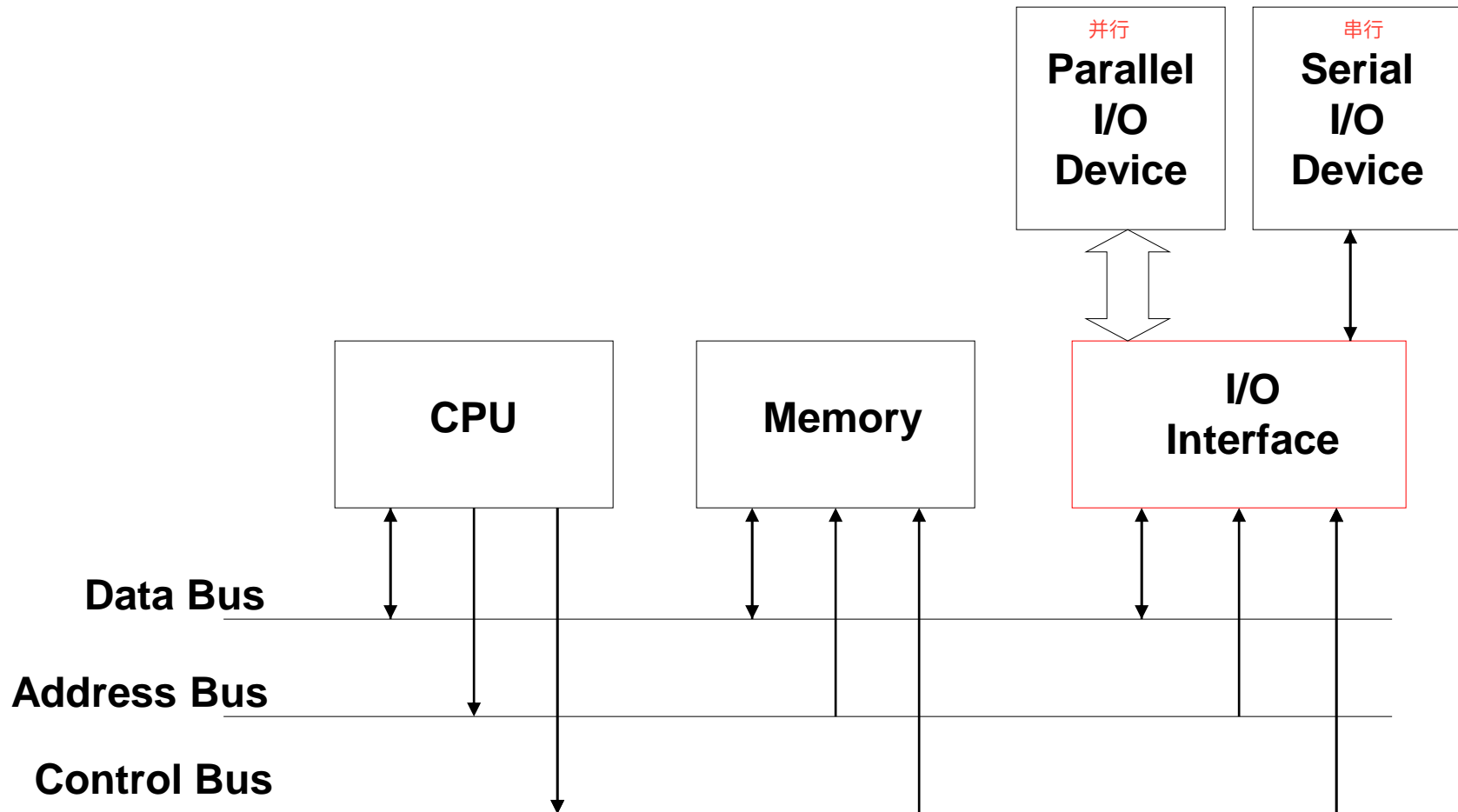


# I/O Addressing

- If the same address bus is used for both memory and I/O, how does hardware distinguish between memory reads/writes and I/O reads/writes?
  - Two approaches:
    - Memory-mapped I/O
    - Separate I/O
  - Both adopted in AVR
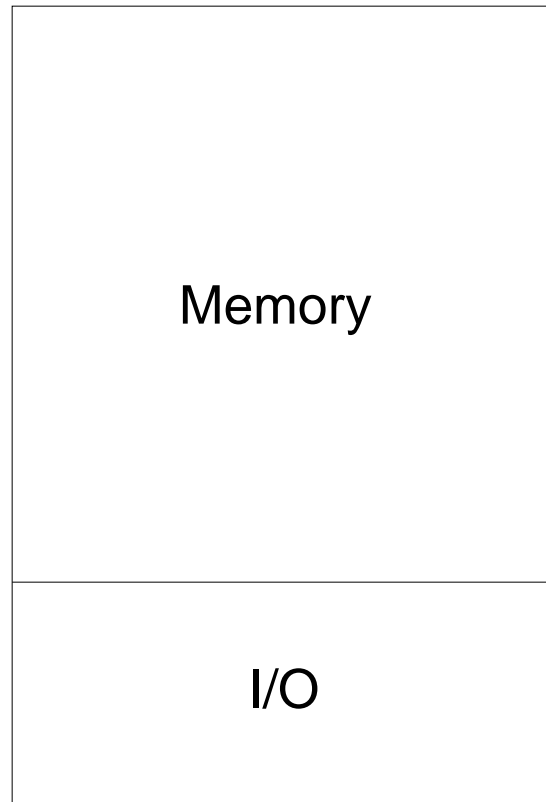
# Memory Mapped I/O

- The entire memory address space contains a section for I/O registers.



# AVR Memory Mapped I/O

- In AVR, 64+ I/O registers are mapped into memory space \$0020 ~ \$01FF
  - with 2-byte address
- With such memory addresses, the access to the I/O's registers uses memory-access type of instructions
  - E.g. *st* and *ld*

	Address (HEX)
32 Registers	0 - 1F
64 I/O Registers	20 - 5F
416 External I/O Registers	60 - 1FF
Internal SRAM (8192 × 8)	200 21FF
External SRAM (0 - 64K × 8)	2200
	FFFF

# Memory Mapped I/O (cont.)

- Advantages:
  - Simple CPU design
  - No special instructions for I/O accesses
  - Scalable
- Disadvantages:
  - I/O devices reduce the amount of memory space available for application programs.
  - The address decoder needs to decode the full address bus to avoid conflict with memory addresses.

# Separate I/O

- Separate address space specifically for I/O.
  - Less expensive address decoders than those needed for memory-mapped I/O
- Special I/O instructions are required.



# Separate I/O (cont.)

- In AVR, the first 64 I/O registers can be addressed with the separate I/O addresses: \$00 ~ \$3F
  - 1-byte addresses
- With such separate addresses, the access to the I/O's registers uses I/O specific instructions.

– *IN* and *OUT*

Address (HEX)	
32 Registers	0 - 1F
64 I/O Registers	20 - 5F
416 External I/O Registers	60 - 1FF
Internal SRAM (8192 × 8)	200 21FF
External SRAM (0 - 64K × 8)	2200
	FFFF

# I/O Synchronization

- CPU is typically much faster than I/O devices.
- Therefore, synchronization between CPU and I/O devices is required.
- Two synchronization approaches:
  - Software
  - Hardware
    - To be covered later

# Software Synchronization

- Two basic methods:
  - Real-time synchronization
    - Uses a software delay to match CPU to the timing requirement of the I/O device.
      - The timing requirement must be known
      - Sensitive to CPU clock frequency
      - Consumes CPU time.
  - Polling I/O
    - A status register, with a DATA\_READY bit, is added to the device. The software keeps reading the status register until the DATA\_READY bit is set.
      - Not sensitive to CPU clock frequency
      - Still consumes CPU time, but CPU can do other tasks at the same time.
- Examples will be given later


# Parallel Input/Output in AVR

- Communication through parallel port
- Two special instructions designed for parallel input/output operations
  - IN
  - OUT
- The port information is given in the next slides.

# Atmega2560

Source: Atmega2560 Data Sheet


## Pin Configuration

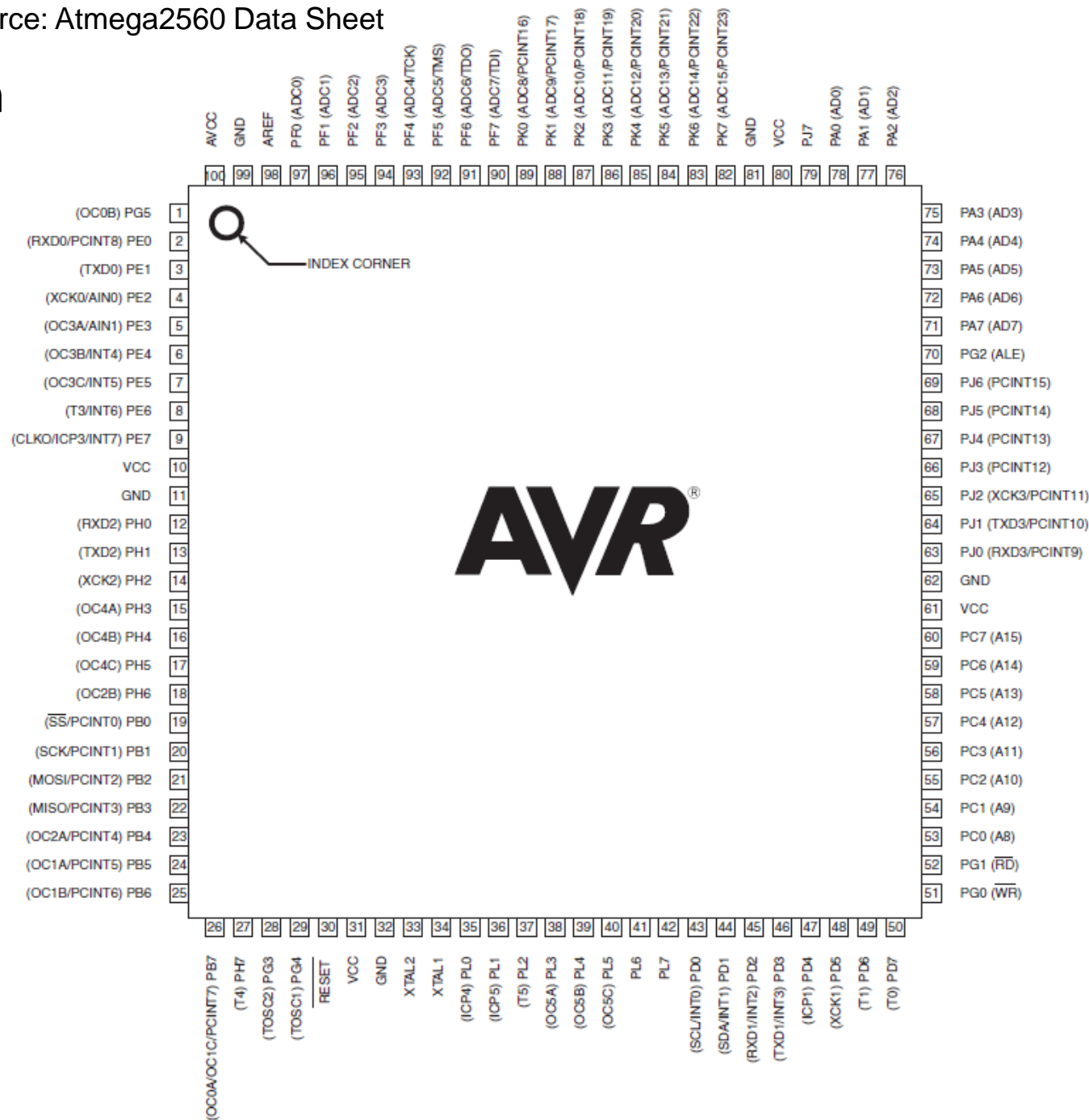

# Atmega2560

## Block Diagram

Source: Atmega2560 Data Sheet

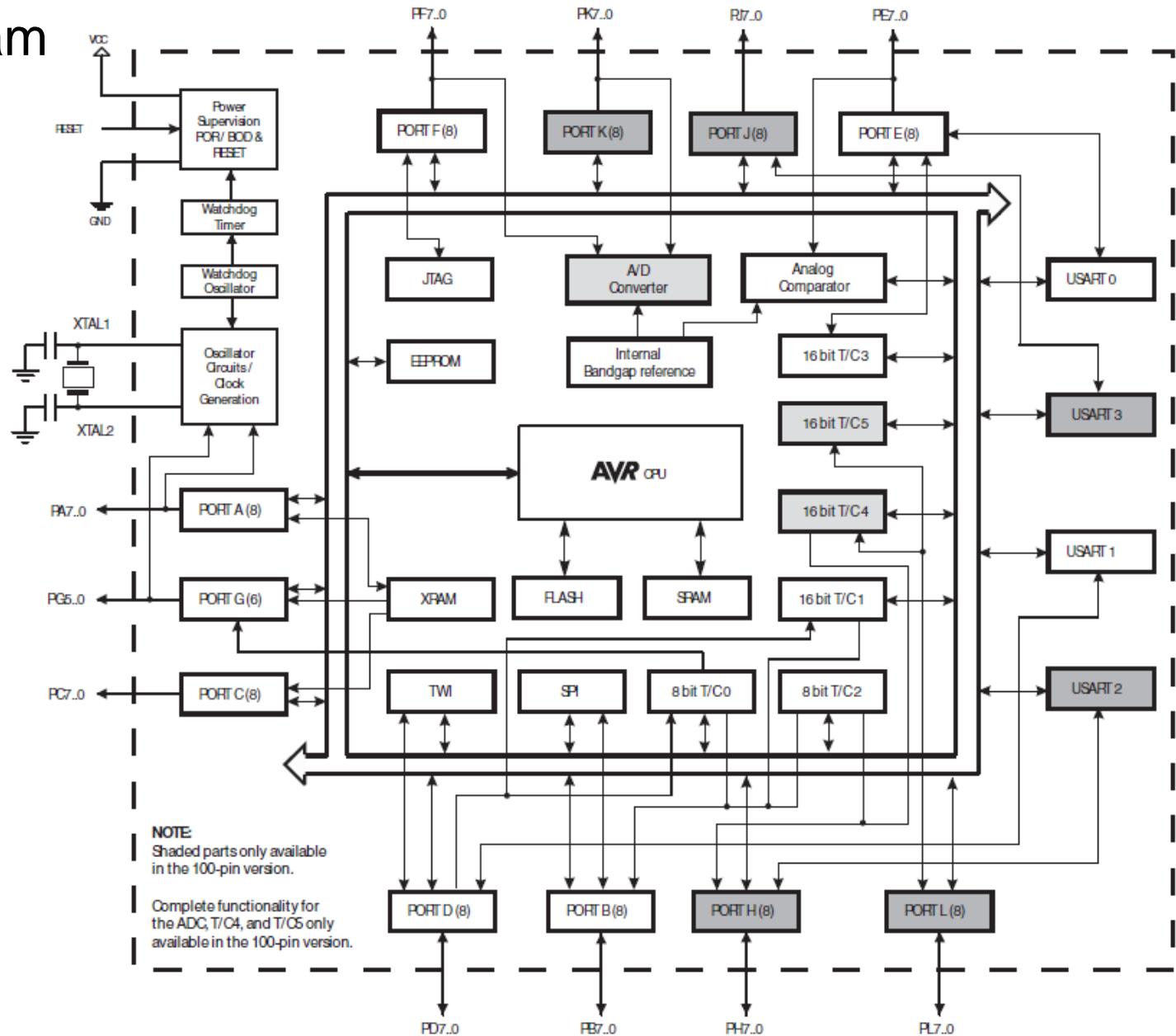

# AVR PORTs

- Can be configured to receive or send data
- Include physical pins and related circuitry to enable input/output operations.
- Different AVR microcontroller devices have different port design
  - ATmega2560 has 100 pins, most of them form ports for parallel input/output.
    - Port A to Port G (7 ports)
      - Having separate I/O addresses
        - » using *in* or *out* instructions
    - Port H to Port L (5 port)
      - Only having memory-mapped addresses
    - Three I/O addresses are allocated for each port. For example, for Port x, the related three registers are:
      - PORTx: data register
      - DDRx: data direction register
      - PINx: input pin register

# Load I/O Data to Register

- Syntax: *in Rd, A*
- Operands:  $0 \leq d \leq 31, 0 \leq A \leq 63$
- Operation:  $Rd \leftarrow I/O(A)$
  
- Words: 1
- Cycles: 1
- Example:  
*in r25, 0x03 ; read port B*




•The names of the I/O ports are given in the device definition file, [m2560def.inc](#).  
•0x03 is an I/O register address of port B



# Store Register Data to I/O Location

- Syntax: *out A, Rr*
- Operands:  $0 \leq r \leq 31, 0 \leq A \leq 63$
- Operation:  $I/O(A) \leftarrow Rr$
  
- Words: 1
- Cycles: 1
- Example:  
*out 0x05, r16 ; write to port B*

# One-bit Port Circuitry\*

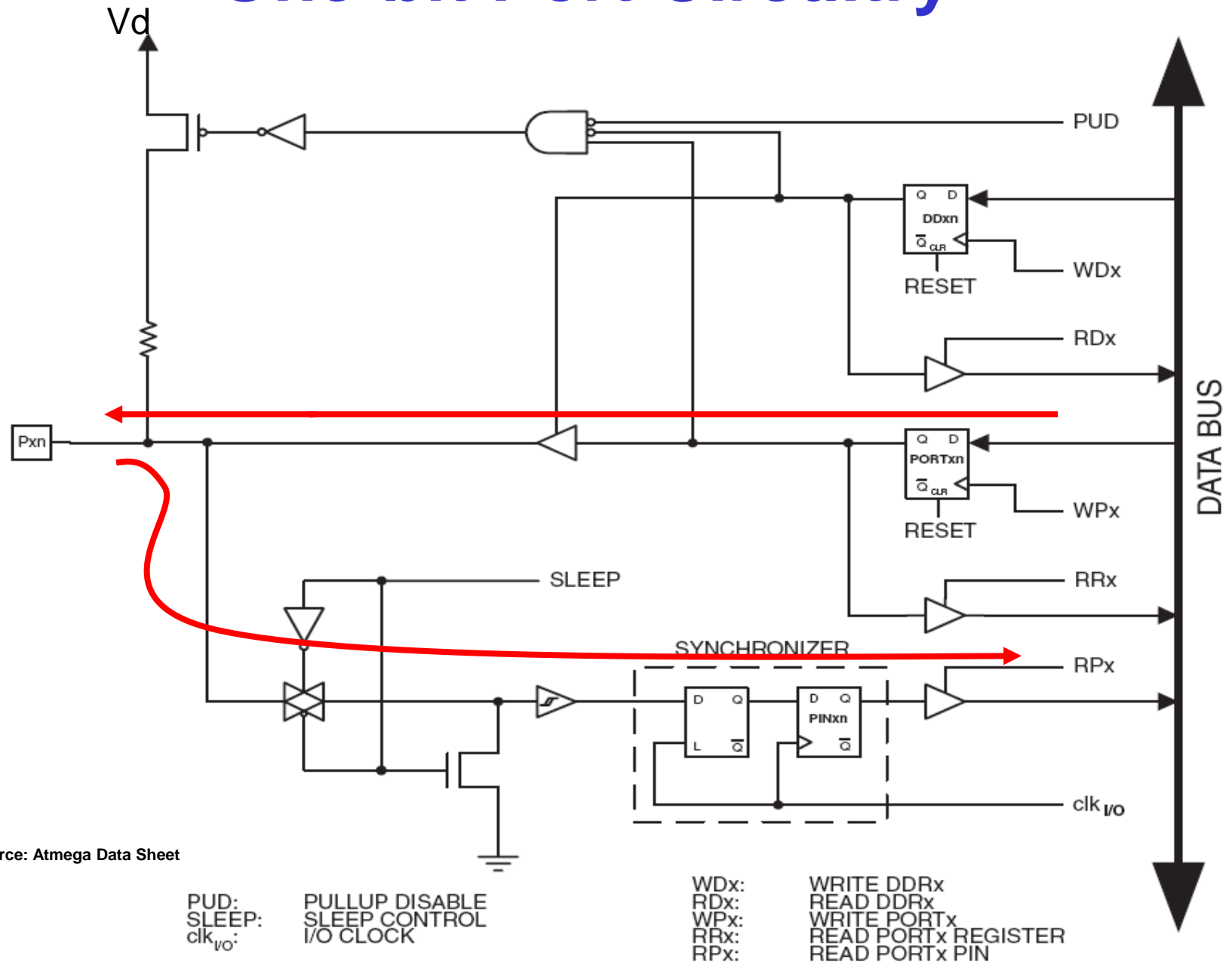

Source: Atmega Data Sheet

# How does it work?\*

- Each one-bit port circuit consists of three register bits. E.g. for pin  $n$  of port  $x$ , we have
  - $DDR_{xn}$ ,  $PORT_{xn}$ , and  $PIN_{xn}$ .
- The  $DDR_{xn}$  bit in the  $DDR_x$  Register selects the direction of this pin.
  - If  $DD_{xn}$  is set to 1, the pin is configured as an output pin. If  $DD_{xn}$  is set to 0, the pin is configured as an input pin.

## How does it work?\* (cont.)

- When the pin is configured as an input pin, the pull-up resistor can be activated/deactivated.
- To active pull-up resistor for input pin, PORTxn needs to be written to 1.

# Sample Code for Output

- PORTx: data register
- DDRx: data direction register
- PINx: input pin register

```
.include "m2560def.inc"
```

```
clr    r16          ; clear r16
ser    r17          ; set r17
out    DDRA, r17    ; set Port A for output operation

out    PORTA, r16   ; write zeros to Port A
nop                    ; wait (do nothing)
out    PORTA, r17   ; write ones to Port A
...
```

# Sample Code for Input

```
.include "m2560def.inc"
```

– PORTx: data register  
– DDRx: data direction register  
– PINx: input pin register


```
    clr      r15  
    out      DDRA, r15      ; set Port A for input operation
```

```
    in       r25, PINA      ; read Port A  
    cpi      r25, 4          ; compare read value with constant  
    breq     exit           ; branch if r25=4
```

```
    ...  
exit:      nop             ; branch destination (do nothing)
```
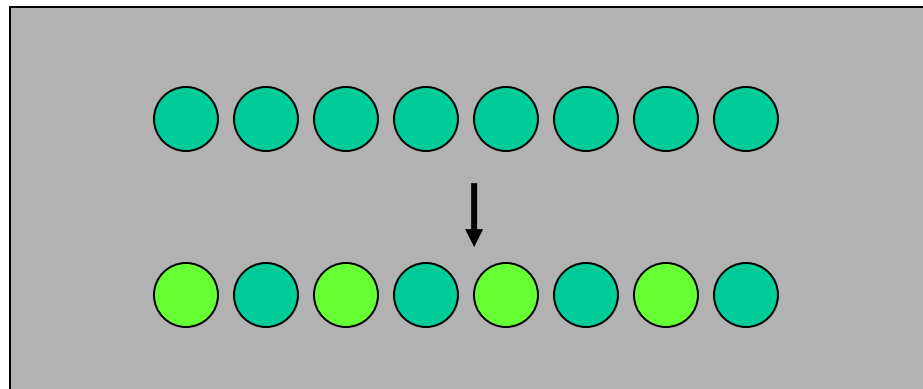
# Example 1


- Design a simple control system that can control a set of LEDs to display a fixed pattern.



•LED: light-emitting diode
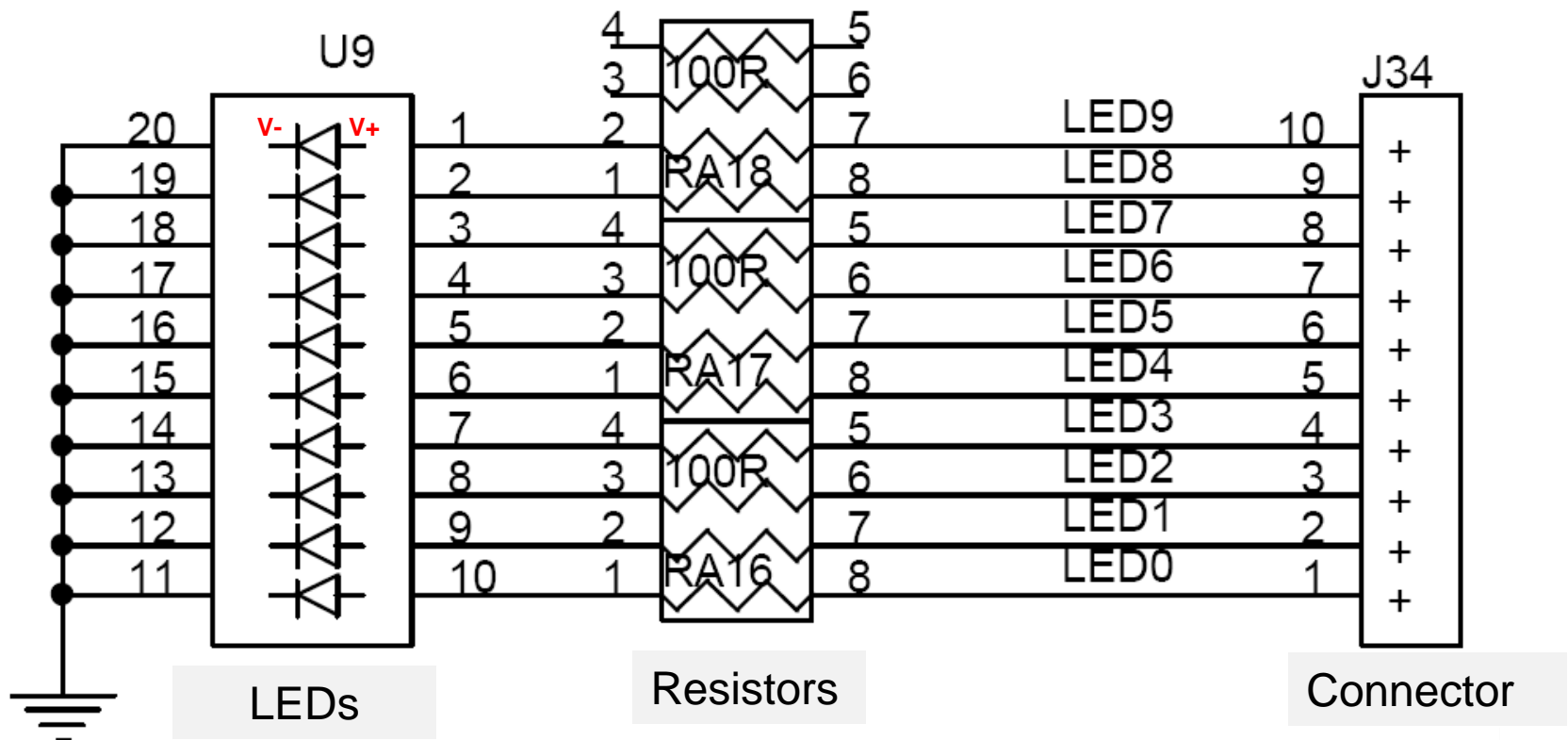
# LED and Its Operation

- For each LED, when its  $V_+ > V_-$ , it will emit light.





# Example 1 (solution)

- The design consists of a number of steps:
  - Set a port for the output operation, one pin of the port is connected to one LED.
  - Write the pattern value to the port so that it drives the LEDs to display the related pattern.


```
.include "m2560def.inc"
    ser r16                ; set all bits in r16 to 1
    out DDRB, r16          ; set Port B for output

    ldi r16, 0xAA          ; write the pattern
    out PORTB, r16

end:
    rjmp end
```
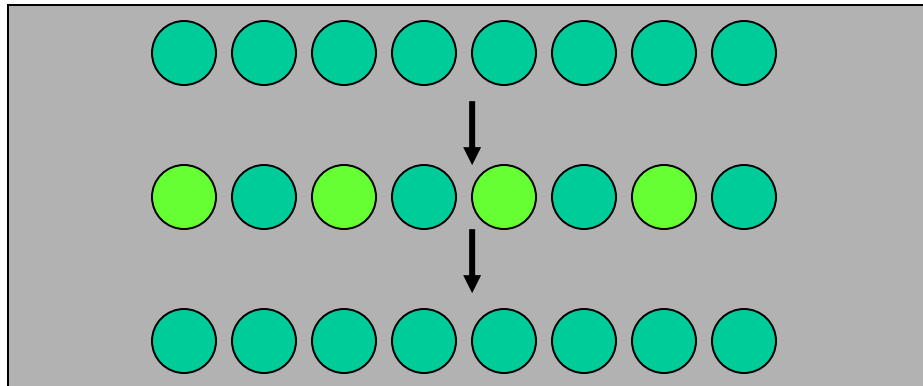
## Example 2

- Design a simple control system that can control a set of LEDs to display a fixed pattern for *one second and then turn the LEDs off.*



## Example 2 (solution)

- The design consists of a number of steps:
  - Set a port for the output operation, one pin of the port is connected to one LED
  - Write the pattern value to the port so that it drives the display of LEDs
  - *Wait for one second*
  - *Write a pattern to set all LEDs off.*

# Counting One Second

- Basic idea:
  - Assume the clock cycle period is 1 ms (very very slow, not a real value). Then we can write a program that executes


$$\frac{1}{10^{-3}} = 1 \times 10^3$$

single-cycle instructions.

- Execution of the code will take 1 second if each instruction in the code takes one clock cycle.
- An AVR implementation example is given in the next slide, **where the 1 ms clock cycle time is assumed.**
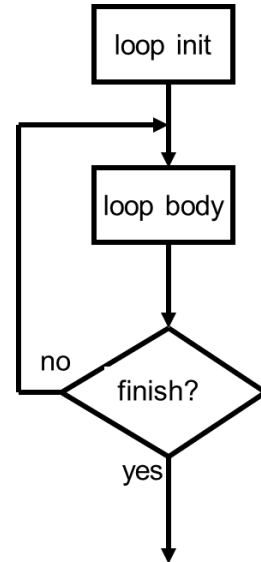
# Code for One Second Delay ( $T_{\text{clock}}=1\text{ms}$ )

```
.include "m2560def.inc"
.equ loop_count = 124
.def iH = r25
.def iL = r24
.def countH = r17
.def countL = r16
.macro oneSecondDelay
    ldi countL, low(loop_count)           ; 1 cycle
    ldi countH, high(loop_count)
    clr iH                                ; 1
    clr iL
loop:  cp iL, countL                       ; 1
      cpc iH, countH
      brsh done                           ; 1, 2 (if branch)
      adiw iH:iL, 1                       ; 2
      nop
      rjmp loop                           ; 2
done:
.endmacro
```



# Code for Example 2

```
.include "m2560def.inc"
```

```
ser r15
```

```
out DDRB, r15           ; set Port B for output
```

```
ldi r15, 0xAA           ; write the pattern
```

```
out PORTB, r15
```

```
oneSecondDelay          ; 1 second delay
```

```
ldi r15, 0x00
```


```
out PORTB, r15          ; turn off the LEDs
```

```
end:
```

```
rjmp end
```
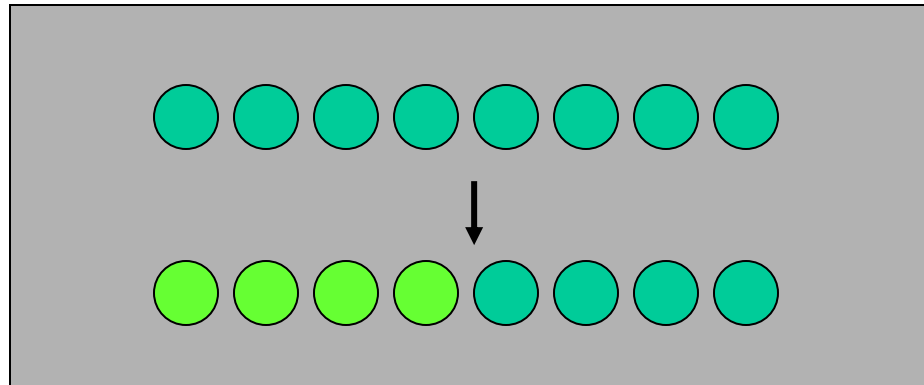
## Example 3

- Design a simple control system that can control a set of LEDs to display a fixed pattern *that is specified by the user.*
  - Assume there are switches. Each switch can provide two possible values (switch-on for logic one and switch-off for logic 0)



# Example 3 (solution)

- Design
  - Connect the switches to the pins of a port
  - Set the port for input
  - Read the input
  - Set another port for the output operation, each pin of the ports is connected to one LED
  - Write the pattern value provided by the input switches to the port so that it drives the display of LEDs
- Execution
  - Set the switches for a desired input value
  - Start the control system



# Code for Example 3

```
.include "m2560def.inc"
```

– PORTx: data register  
– DDRx: data direction register  
– PINx: input pin register

```
clr r17
```

```
out DDRC, r17
```

```
; set Port C for input
```

```
ser r17
```

```
out PORTC, r17
```

```
; activate the pull up
```

```
in r17, PINC
```

```
; read the pattern set by the user  
; from the switches
```

```
ser r16
```

```
out DDRB, r16
```

```
; set Port B for output
```

```
out PORTB, r17
```

```
; write the input pattern
```

```
end:
```

```
rjmp end
```


## Example 4

- Design a simple control system that can control a set of LEDs to display a pattern specified by the user *during the execution*.

## Example 4 (solution)

- Using polling to handle dynamic input
  - The processor continues checking if there is an input for read. If there is, the processor reads the input and goes to next task, otherwise the processor is in a waiting state for the input.

# Example 4 (solution)

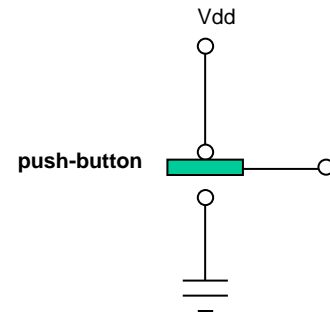

- Design
  - Set one port for input and connect each pin of the port to one switch
  - Set another port for the output operation, each pin of the ports is connected to one LED
  - Set a pin for input and connect the pin to the push-button,
    - When the button is pressed, it signals “Input Pattern is ready”
  - Poll the pin until “Input Pattern is ready”
  - Read the input pattern
  - Write the pattern to the port so that it drives the display of LEDs
- During execution
  - Set the switches for the input value
  - Push the button
  - The LEDs show the pattern as specified by the user.

# Code for Example 4

- Set an extra input bit for signal from user when the input is ready.

```
.include "m2560def.inc"
```

– PORTx: data register  
– DDRx: data direction register  
– PINx: input pin register

```
    cbi DDRD, 7                                ; set Port D bit 7 for input
```

```
    clr r17
```

```
    out DDRC, r17                              ; set Port C for input
```

```
    ser r17
```

```
    out PORTC, r17                             ; activate the pull up 激活电阻
```

```
    out DDRB, r17                              ; set Port B for output
```

```
waiting:
```

```
    sbic PIND, 7                                ; check if that bit is clear
```

I/O位清零跳行

```
    rjmp waiting                              ; if yes skip the next instruction
```

```
    ; waiting
```

```
    in r17, PINC                               ; read pattern set by the user
```

```
    ; from the switches
```

```
    out PORTB, r17
```

```
    rjmp waiting
```

# Reading Materials

- Chapter 9: Computer Buses and Parallel Input and Output. Microcontrollers and Microcomputers by Fredrick M. Cady.
- Mega2560 Data Sheet
  - Ports

# Homework

1. Refer to the AVR Instruction Set manual, study the following instructions:
  - Arithmetic and logic instructions
    - `ser`
  - Data transfer instructions
    - `in, out`
  - Bit operations
    - `sbi, cbi`
  - Program control instructions
    - `sbic, sbis`
  - MCU control instructions
    - `nop`

# Homework

2. Refer to “Introduction to Lab Board”. Study the lab board. Write the assembly code to display pattern 10110111 on the LED bar through each of the following I/O ports:
- (a) port C
  - (b) port F
  - (c) port L



# Homework

## 3. Study the following code. What is its function ?

```
.equ PATTERN1 = 0x5B
.equ PATTERN2 = 0xAA

    ser temp
    out DDRC, temp           ; PORTC is output
    out PORTC, temp         ; Write ones to all the LEDs
    out PORTF, temp         ; Enable pull-up resistors on PORTF
    clr temp
    out DDRF, temp          ; PORTF is input
switch0:
    sbic PINF, 0            ; Check push button PB0
    rjmp switch1            ; If not pushed, check the other push button PB1
    ldi temp, PATTERN1
    out PORTC, temp         ; If PB0 pushed, display PATTERN1
switch1:
    sbic PINF, 1            ; Check push button PB1
    rjmp switch0            ; If not pushed, check the other switch PB0
    ldi temp, PATTERN2
    out PORTC, temp         ; If PB1 pushed, display PATTERN2
    rjmp switch0            ; Now check PB0 again
```